



Sri

SAI RAM
ENGINEERING COLLEGE
INSTITUTE OF TECHNOLOGY

West Tambaram, Chennai - 44

YEAR

II

SEM

III

CS 8351

DIGITAL PRINCIPLES AND SYSTEM DESIGN
(Common to CSE & IT)

UNIT NO.3


3.3 ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

Version: 1.0

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

SEQUENTIAL CIRCUITS

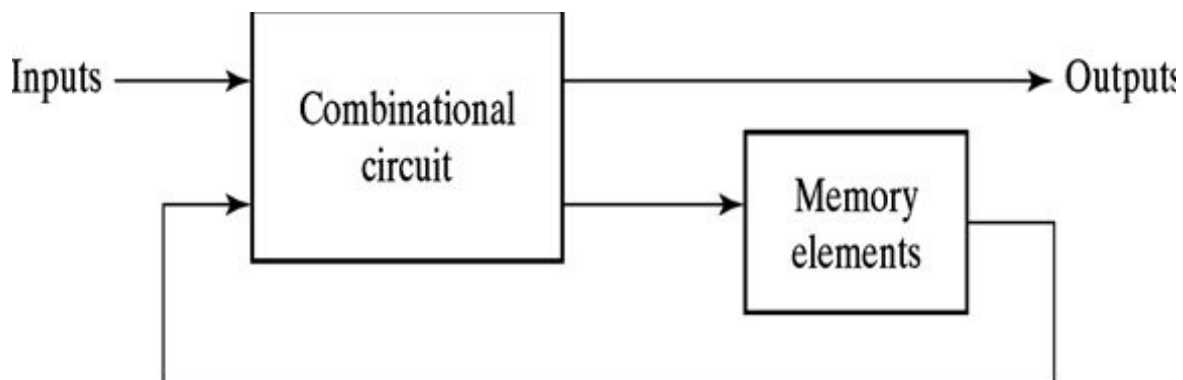- Consist of a combinational circuit to which storage elements are connected to form a feedback path
- State – the state of the memory devices now, also called **current state**
- Next states and outputs are functions of inputs and present states of storage elements



SEQUENTIAL CIRCUIT ANALYSIS


- The behavior of a clocked sequential circuit is determined from
 - The inputs
 - The outputs
 - The state of its flip-flops
 - The outputs and the next state are both a function of the inputs and the present state
 - To analyze a sequential circuit, we can use
 - State equations
 - State table
 - State diagram
 - Flip-Flop input equations

STATE EQUATIONS

- Specify the next state as a function of present state and inputs.
- Also called transition equation.

- Analyze the combinational part directly

Consider the logic diagram:

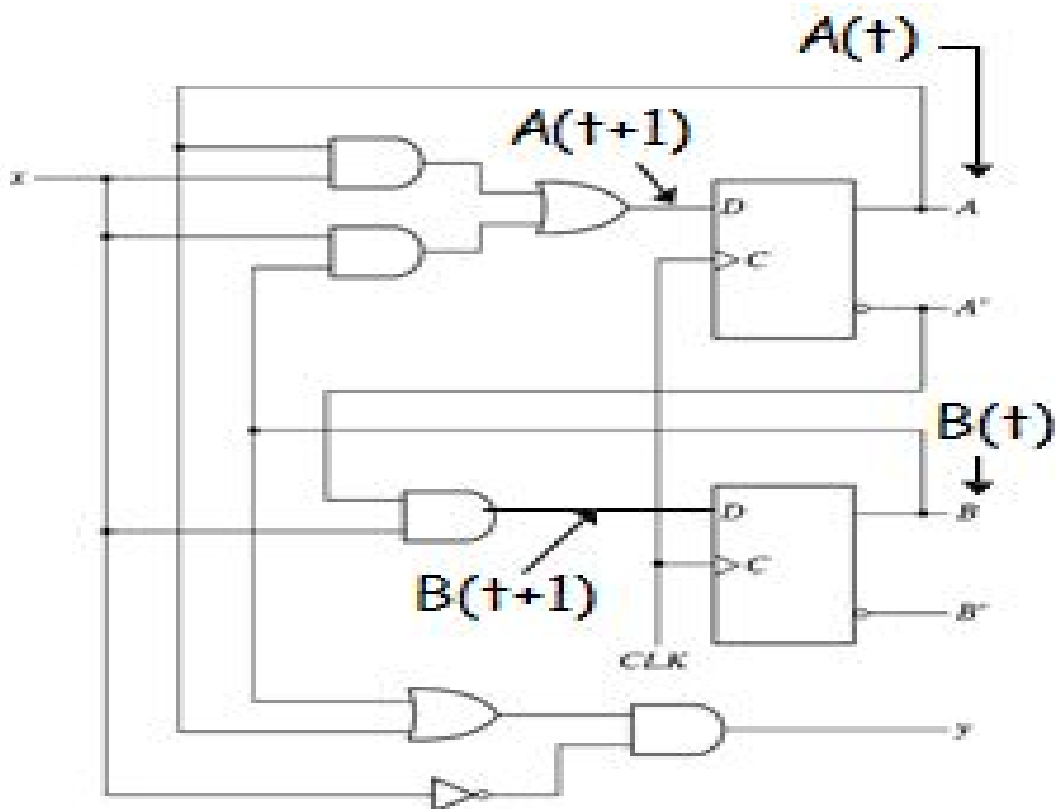

EX:

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$A(t+1) = Ax + Bx$$

$$B(t+1) = A'(t) x(t)$$

$$(ie) B(t+1) = A'x$$

$$y(t)=[A(t)+B(t)] x(t)$$

$$(ie) y=(A+B)x'$$

STATE TABLE

- Enumerate the time sequence of inputs, outputs, and flip-flop states
 - Also called transition table
 - Similar to list the truth table of state equations
- Consist of four sections
 - Present state, input, next state, and output
- A sequential circuit with m flip-flops and n inputs need 2^{m+n} rows in the state table

Present state		input	Next state		output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


SECOND FORM OF STATE TABLE

- The state table has only three section: present state, next state, and output
- The input conditions are enumerated under next state and output sections

Present State		Next State				Output	
		X=0		X=1		X=0	X=1
A	B	A	B	A	B	Y	Y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

STATE DIAGRAM

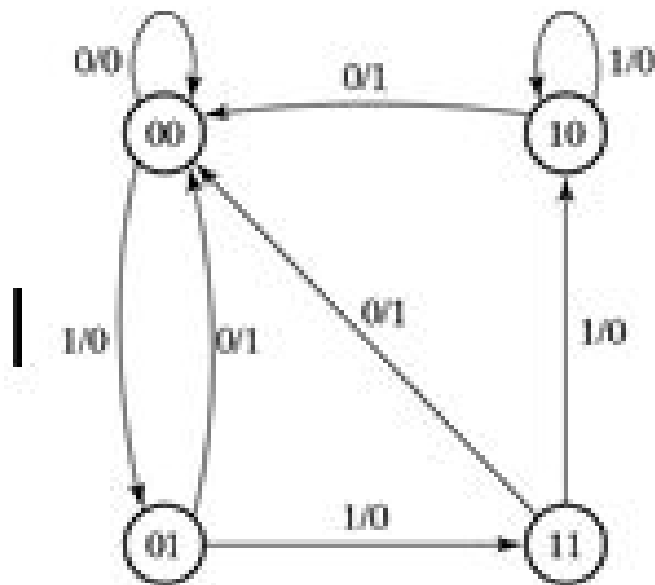- Graphically represent the information in a state table
 - Circle: a state (with its state value inside)
 - Directed lines: state transitions (with inputs/outputs above)
- Ex: starting from state 00
 - If the input is 0, it stays at state 00 with output=0
 - If the input is 1, it goes to state 01 with output=0



FLIP-FLOP INPUT EQUATIONS

- To draw the logic diagram of a sequential circuit, we need
 - The type of flip-flops
 - A list of Boolean expressions of the combinational circuits
- The Boolean functions for the circuit that generates external outputs is called output equations
- The Boolean functions for the circuit that generates the inputs to flip-flops is flip-flop input equations
- Sometimes called excitation equations
- The flip-flop input equations provide a convenient form for specifying the logic diagram of a sequential circuit

Input: $D_A = Ax + Bx$


$D_B = A'x$

Output: $y = (A + B)x'$

ANALYSIS WITH OTHER FLIP-FLOPS

- The sequential circuit using other flip-flops such as JK or T type can be analyzed as follows
- Determine the flip-flop input equations in terms of the present state and input variables
- List the binary values of each input equation
- Use the corresponding flip-flop characteristic table to determine the state values in the state table

ANALYSIS WITH JK FLIP-FLOPS (1/2)

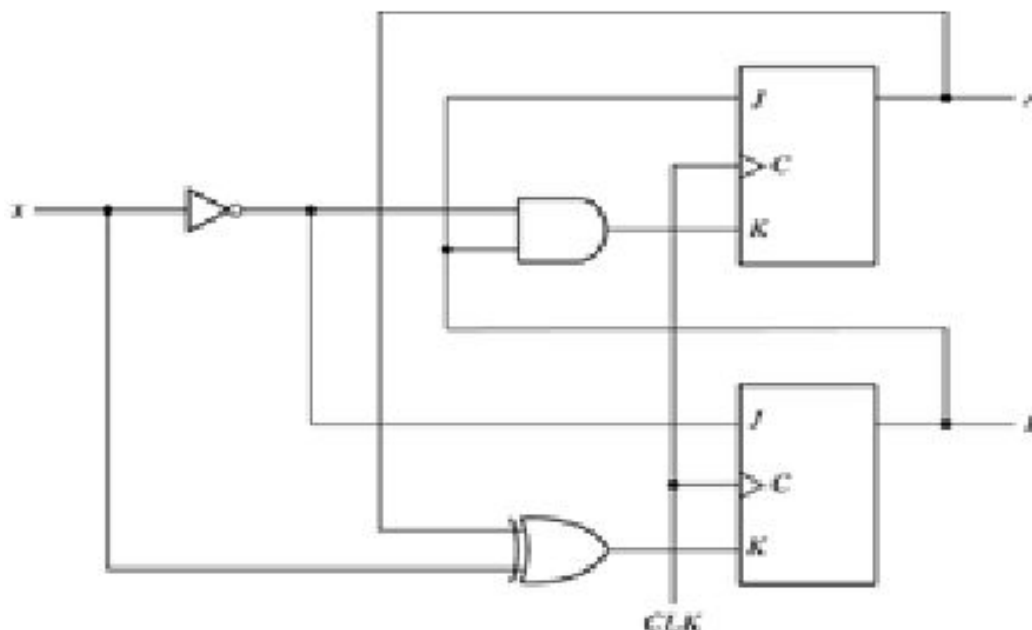

Step 1: input equations

$$J_A = B,$$

$$K_A = Bx'$$

$$J_B = x'$$

$$K_B = A \oplus x'$$

Step 2: state equations

$$A(t+1) = JA' + K'A$$

$$= BA' + (Bx')'A$$

$$= A'B + AB' + Ax$$

$$B(t+1) = JB' + K'B$$


$$= x'B' + (A \oplus x)'B$$

$$B(t+1) = B'x' + ABx + A'Bx'$$


STEP 3: STATE TABLE

Present state		Input	Next state		Flip-Flop Inputs			
A	B	X	A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

STEP 4: STATE DIAGRAM

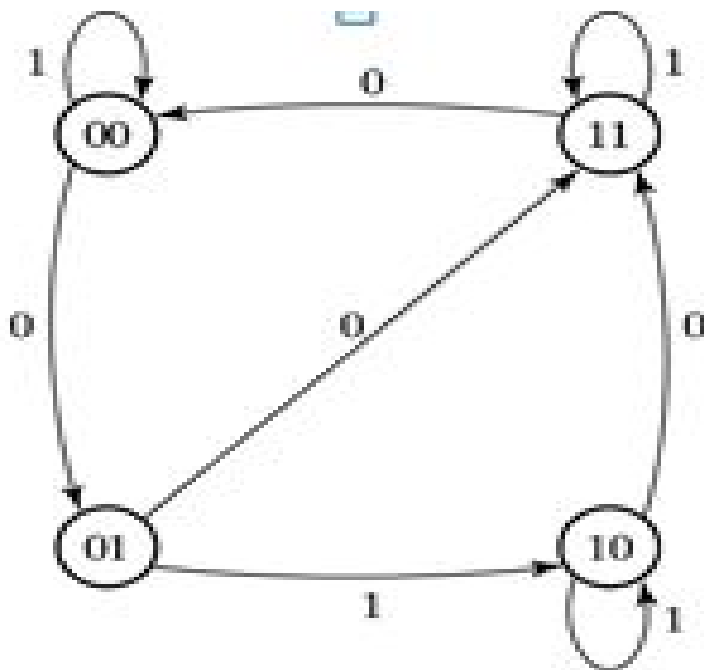

ANALYSIS WITH T FLIP-FLOPS (1/2)

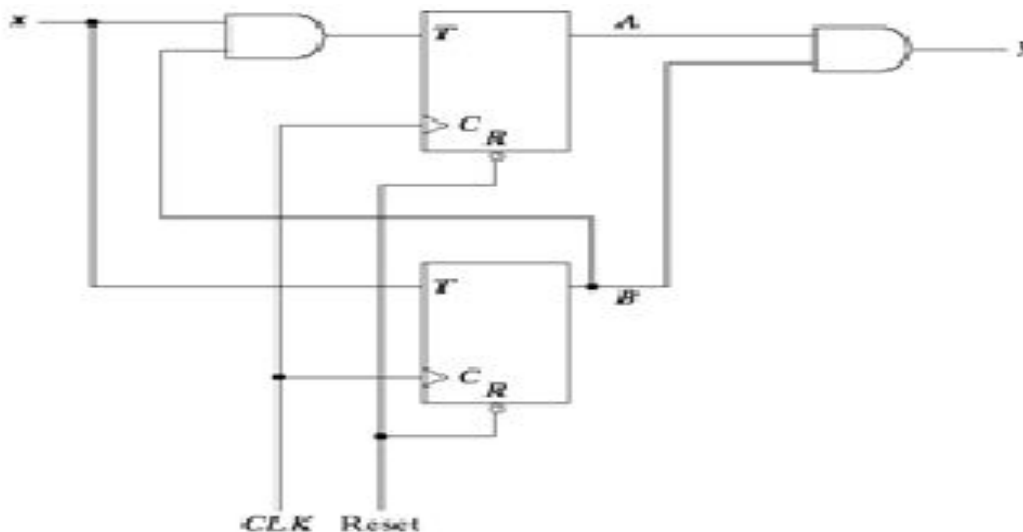

Step 1: input equations

$$T_A = Bx$$

$$T_B = x$$

$$y = AB$$

Step 2: state equations

$$\begin{aligned} A(t+1) &= T'A + TA' \\ &= (Bx)'A + (Bx)A' \\ &= AB' + Ax' + A'Bx \end{aligned}$$

$$B(t+1) = T'B + TB'$$


DIGITAL PRINCIPLES AND SYSTEM DESIGN
(Common to CSE & IT)

$$= x'B + xB'$$

$$= x \oplus B$$

STEP 3: STATE TABLE


Present state		Input	Next state		Output
A	B	X	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

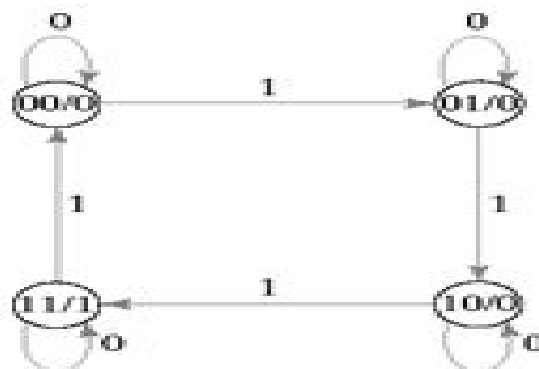STEP 4: STATE DIAGRAM

MEALY AND MOORE MODEL

■ Mealy model :

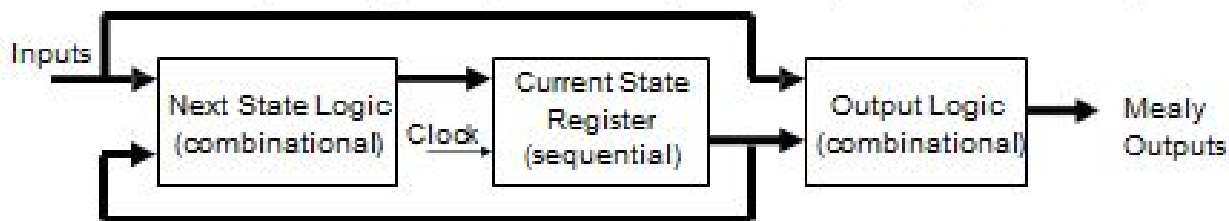- The output is a function of **both** the present state and input
- The output may change if the inputs change during a clock cycle



MOOREMODEL

The output is a function of the **present state only**

The output are **synchronized** with the clock

