



Sai
SAI RAM
ENGINEERING COLLEGE
INSTITUTE OF TECHNOLOGY

West Tambaram, Chennai - 44



YEAR	SEM
II	III

CS 8351

DIGITAL PRINCIPLES AND SYSTEM DESIGN
(Common to CSE & IT)

UNIT NO. III

3.8 HDL Models of Sequential circuits

Version: 1.0



HDL MODELS

The Verilog HDL model can be described in any one of the following modeling styles,

- ✓ Gate level modeling-using instantiations of predefined and user defined primitive gates.
- ✓ Dataflow modeling using continuous assignment with the keyword **assign**.
- ✓ Behavioral modeling using procedural assignment statements with the keyword **always**.

➤ Gate level modeling

In this type, a circuit is specified by its logic gates and their interconnections. Gate level modeling provides a textual description of a schematic diagram. The verilog HDL includes 12 basic gates as predefined primitives. They are and, nand, or, nor, xor, xnor, not & buf.

HDL

```
// Gate-level description of two-to-four-line decoder
// Refer to Fig. 4.19 with symbol E replaced by enable, for clarity.

module decoder_2x4_gates (D, A, B, enable);
    output      [0: 3]    D;
    input       A, B;
    input       enable;
    wire        A_not, B_not, enable_not;

    not
        G1 (A_not, A),
        G2 (B_not, B),
        G3 (enable_not, enable);
    nand
        G4 (D[0], A_not, B_not, enable_not),
        G5 (D[1], A_not, B, enable_not),
        G6 (D[2], A, B_not, enable_not),
        G7 (D[3], A, B, enable_not);
endmodule
```

➤ **Dataflow modeling**

Dataflow modeling of combinational logic uses a number of operators that act on operands to produce desired results. Verilog HDL provides about 30 different operators. Dataflow modeling uses continuous assignments and the keyword **assign**. A continuous assignment is a statement that assigns a value to a net. The data type family **net** is used to represent a physical connection between circuit elements.

Some Verilog HDL Operators	
Symbol	Operation
+	binary addition
-	binary subtraction
&	bitwise AND
	bitwise OR
^	bitwise XOR
~	bitwise NOT
==	equality
>	greater than
<	less than
{ }	concatenation
?:	conditional

HDL for 2-to-4 line decoder

```
module decoder_2x4_df (
    output [0:3] D,
    input A, B,
    enable
);

    assign D[0] = ~(~A & ~B & ~enable),
           D[1] = ~(~A & B & ~enable),
           D[2] = ~(A & ~B & ~enable),
           D[3] = ~(A & B & ~enable);

endmodule
```

➤ Behavioral modeling

Behavioral modeling represents digital circuits at a functional and algorithmic level. It is used mostly to describe sequential circuits, but can also be used to describe combinational circuits. Behavioral descriptions use the keyword **always**, followed by an optional event control expression and a list of procedural assignment statements.

```
// Behavioral description of two-to-one-line multiplexer  
module mux_2x1_beh (m_out, A, B, select);  
  output      m_out;  
  input       A, B, select;  
  reg         m_out;  
  
  always      @(A or B or select)  
    if (select == 1) m_out = A;  
    else m_out = B;  
endmodule
```