



*Sai*  
**SAI RAM**  
ENGINEERING COLLEGE  
INSTITUTE OF TECHNOLOGY

West Tambaram, Chennai - 44

YEAR	SEM
II	III

**CS8351**

Digital Principles and System Design  
(Common to CSE and IT)

## UNIT III SYNCHRONOUS SEQUENTIAL LOGIC

### 3.6 REGISTERS

## REGISTERS

A register is simply a group of Flip-Flops that can be used to store a binary number. There must be one Flip-Flop for each bit in the binary number. For instance, a register used to store an 8-bit binary number must have 8 Flip-Flops.

The Flip-Flops must be connected such that the binary number can be entered (shifted) into the register and possibly shifted out. A group of Flip-Flops connected to provide either or both of these functions is called a ***shift register***.

The bits in a binary number (data) can be removed from one place to another in either of two ways. The first method involves shifting the data one bit at a time in a serial fashion, beginning with either the most significant bit (MSB) or the least significant bit (LSB). This technique is referred to as *serial shifting*. The second method involves shifting all the data bits simultaneously and is referred to as *parallel shifting*.

There are two ways to shift into a register (serial or parallel) and similarly two ways to shift the data out of the register.


### Shift Registers

**A register that moves the binary information from one flip flop to its neighboring flip flop upon the occurrence of a clock pulse is called shift register.** The movement data may be unidirectional (left or right) or bidirectional (serial or parallel). Based on the manner in which data is entered into the register and come out from the register, the registers are broadly categorized into four types.

- **Serial In Serial Out (SISO)**
- **Serial In Parallel Out (SIPO)**
- **Parallel In Serial Out (PISO)**
- **Parallel In Parallel Out (PIPO)**

A shift register is a sequential circuit which stores the data and shifts it towards the output on every clock cycle.

- **Serial-in to Parallel-out (SIPO)** - the register is loaded with serial data, one bit at a time, with the stored data being available at the output in parallel form.
- **Serial-in to Serial-out (SISO)** - the data is shifted serially “IN” and “OUT” of the register, one bit at a time in either a left or right direction under clock control.
- **Parallel-in to Serial-out (PISO)** - the parallel data is loaded into the register simultaneously and is shifted out of the register serially one bit at a time under clock control.
- **Parallel-in to Parallel-out (PIPO)** - the parallel data is loaded simultaneously into the register, and transferred together to their respective outputs by the same clock pulse.

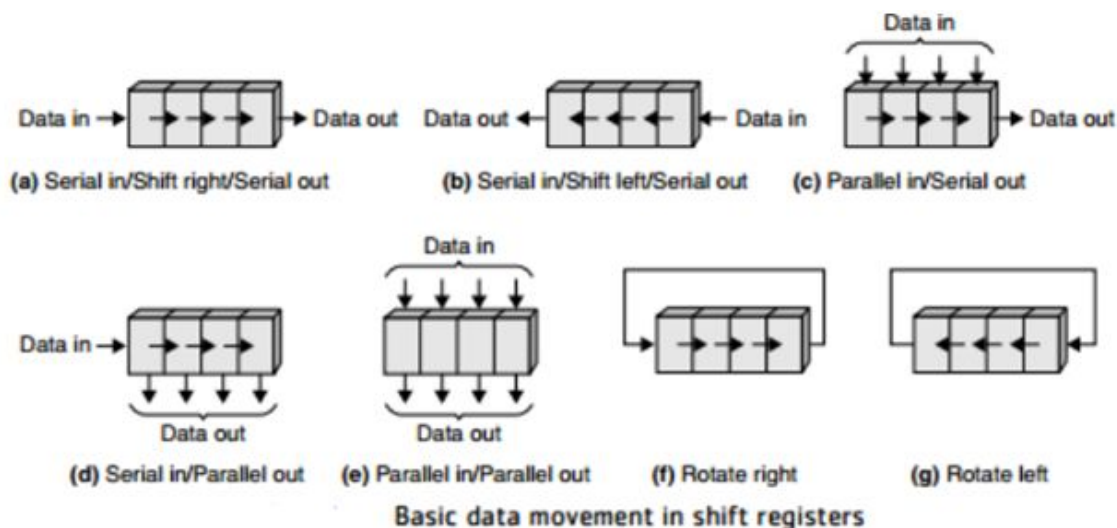


### Applications of shift Registers –

- The shift registers are used for temporary data storage.
- The shift registers are also used for data transfer and data manipulation.

- The serial-in serial-out and parallel-in parallel-out shift registers are used to produce time delay to digital circuits.
- The serial-in parallel-out shift register is used to convert serial data into parallel data thus they are used in communication lines where demultiplexing of a data line into several parallel line is required.
- A Parallel in Serial out shift register used to convert parallel data to serial data.
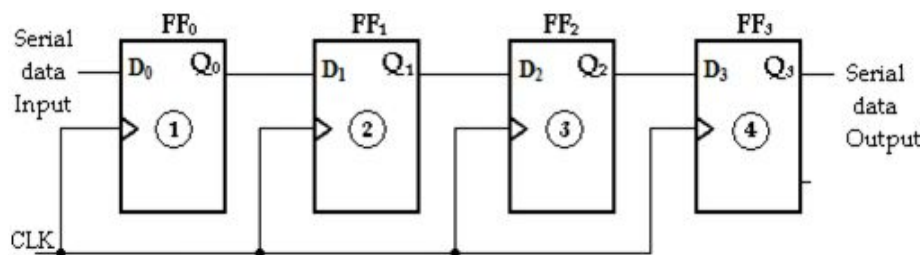
### Serial-In Serial-Out Shift Register:

The serial in/serial out shift register accepts data serially, i.e., one bit at a time on a single line. It produces the stored information on its output also in serial form.




Serial-In Serial-Out Shift Register


The entry of the four bits 1010 into the register is illustrated below, beginning with the right-most bit. The register is initially clear. The 0 is put onto the data input line, making  $D=0$  for FF0. When the first clock pulse is applied, FF0 is reset, thus storing the 0.

Next the second bit, which is a 1, is applied to the data input, making  $D=1$  for FF0 and  $D=0$  for FF1 because the D input of FF1 is connected to the Q0 output. When the second clock pulse occurs, the 1 on the data input is shifted into FF0, causing FF0 to set; and the 0 that was in FF0 is shifted into FF1.

The third bit, a 0, is now put onto the data-input line, and a clock pulse is applied. The 0 is entered into FF0, the 1 stored in FF0 is shifted into FF1, and the 0 stored in FF1 is shifted into FF2.

The last bit, a 1, is now applied to the data input, and a clock pulse is applied. This time the 1 is entered into FF0, the 0 stored in FF0 is shifted into FF1, the 1 stored in FF1 is shifted into FF2, and the 0 stored in FF2 is shifted into FF3. This completes the serial entry of the four bits into the shift register, where they can be stored for any length of time as long as the Flip-Flops have dc power.

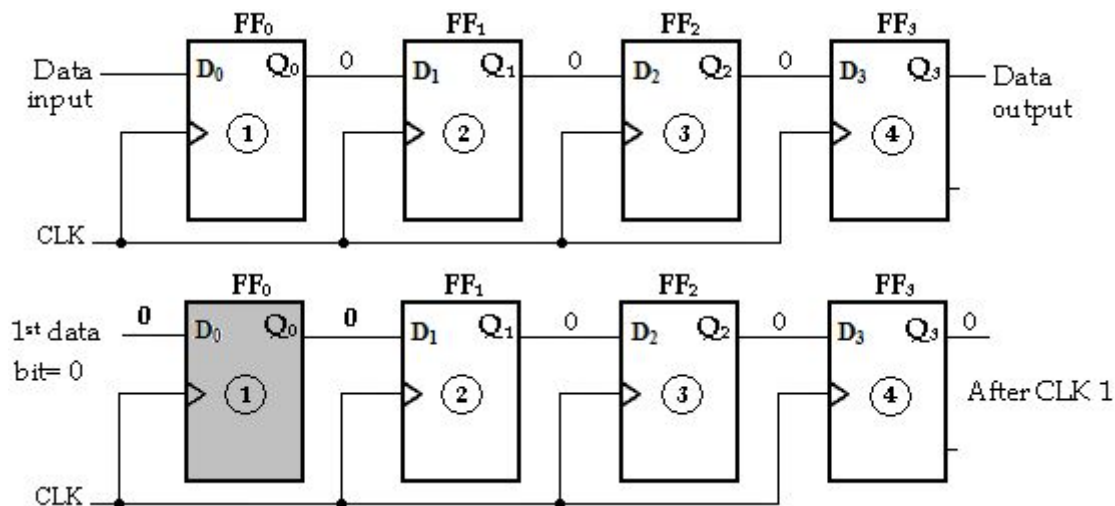

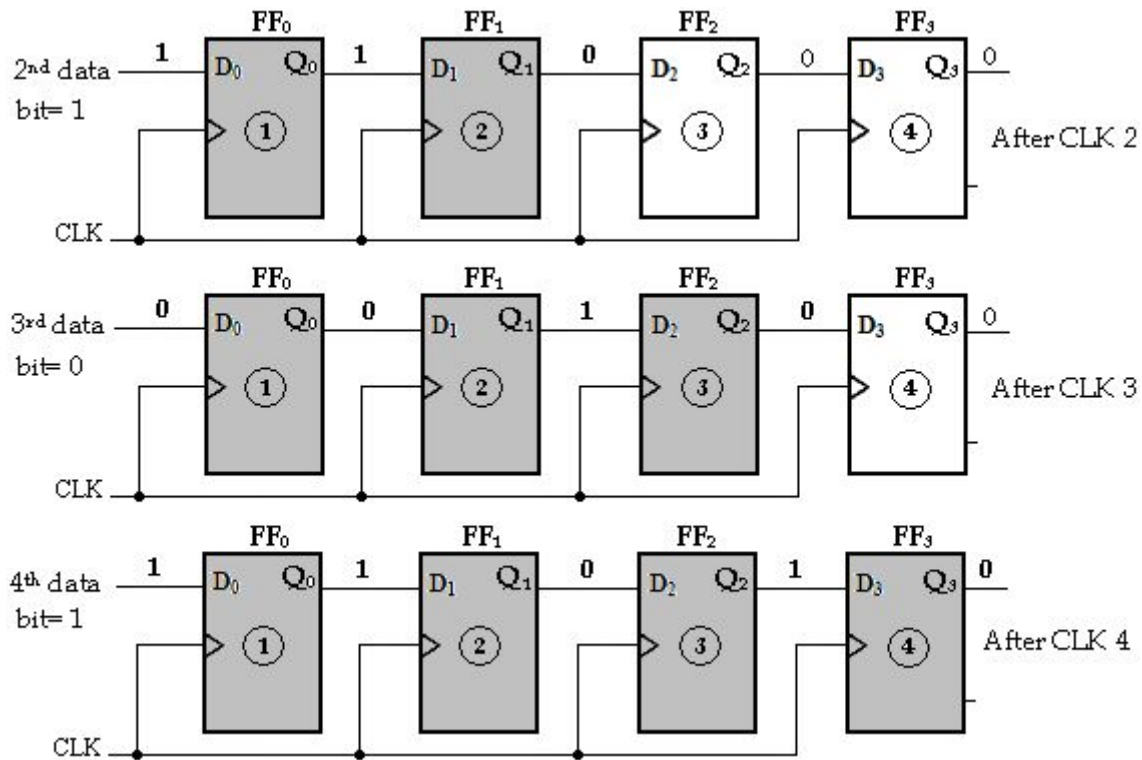


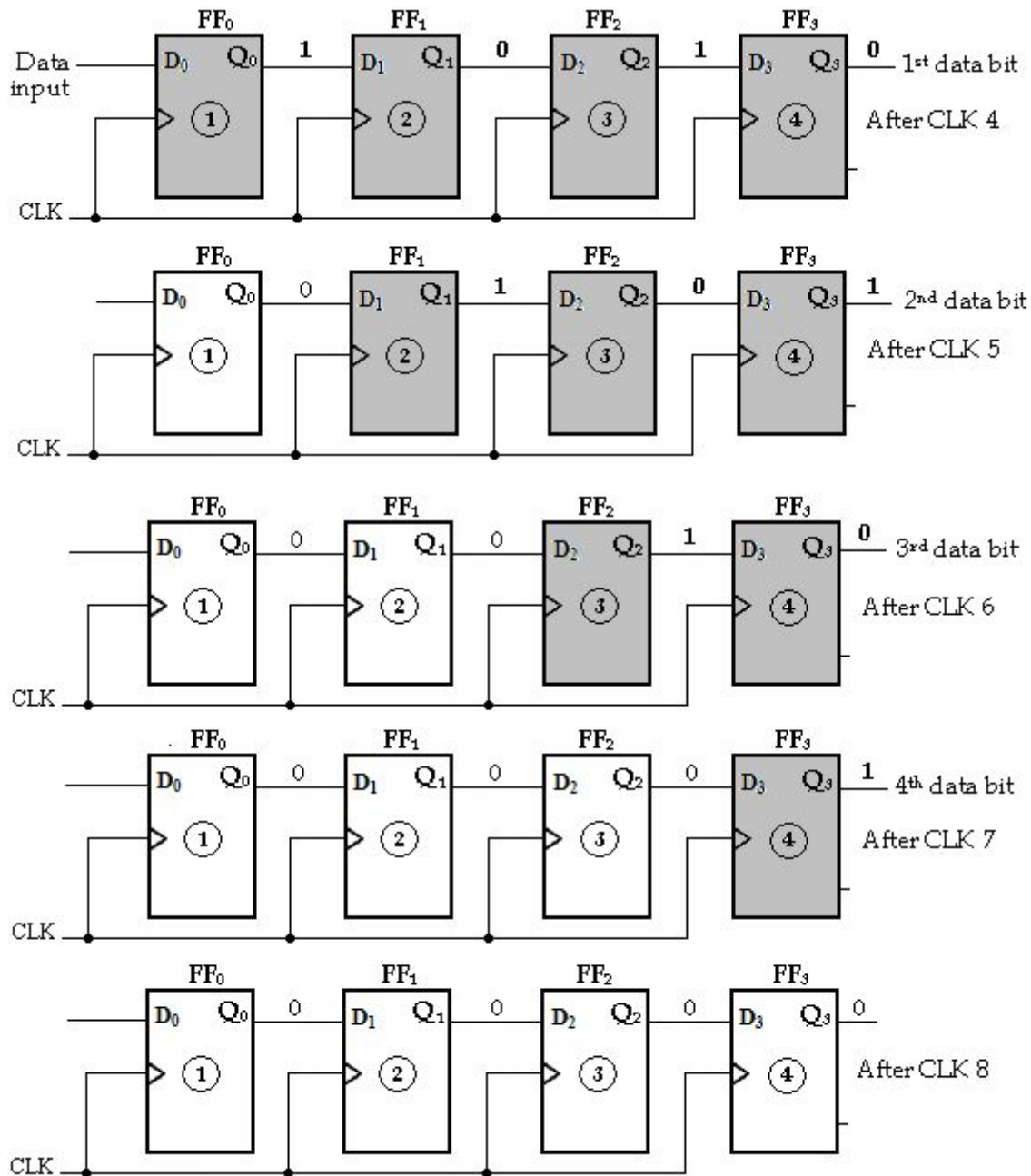**Four bits (1010) being entered serially into the register**

To get the data out of the register, the bits must be shifted out serially and taken off the Q<sub>3</sub> output. After CLK<sub>4</sub>, the right-most bit, 0, appears on the Q<sub>3</sub> output.

When clock pulse CLK<sub>5</sub> is applied, the second bit appears on the Q<sub>3</sub> output. Clock pulse CLK<sub>6</sub> shifts the third bit to the output, and CLK<sub>7</sub> shifts the fourth bit to the output. While the original four bits are being shifted out, more bits can be shifted in. All zeros are shown being shifted out, more bits can be shifted in.






Four bits (1010) being entered serially-shifted out of the register and replaced by all zeros

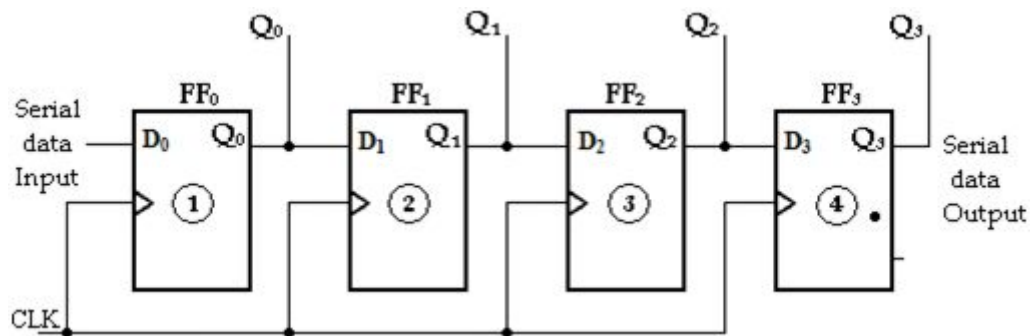
## Serial-In Parallel-Out Shift Register:

In this shift register, data bits are entered into the register in the same as serial-in serial-out shift register. But the output is taken in


parallel. Once the data are stored, each bit appears on its respective output line and all bits are available simultaneously instead of on a bit-by-bit.



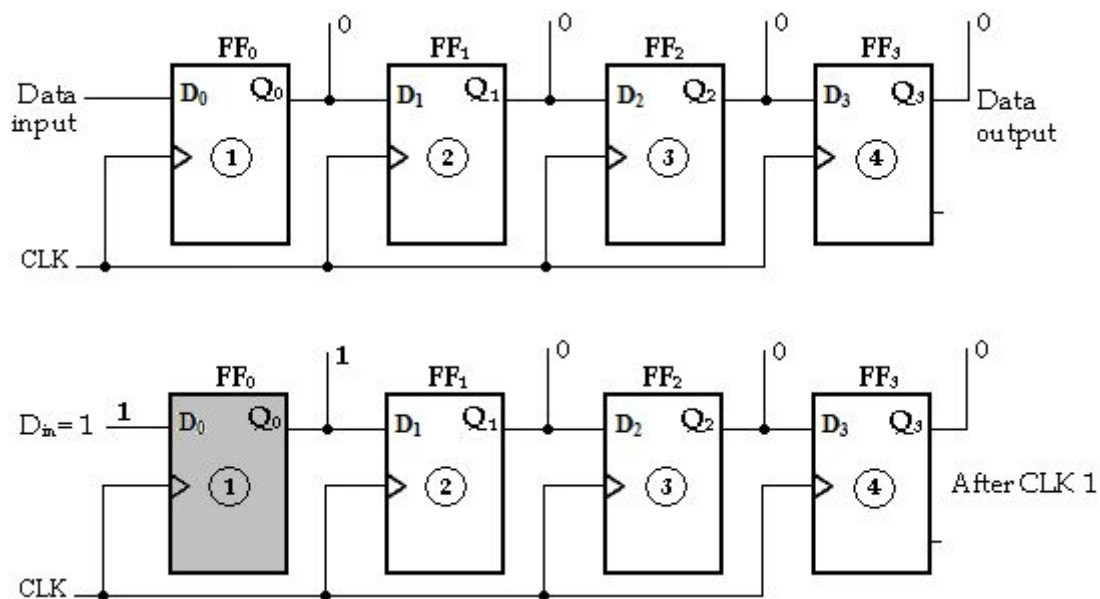**Serial-In parallel-Out Shift Register**





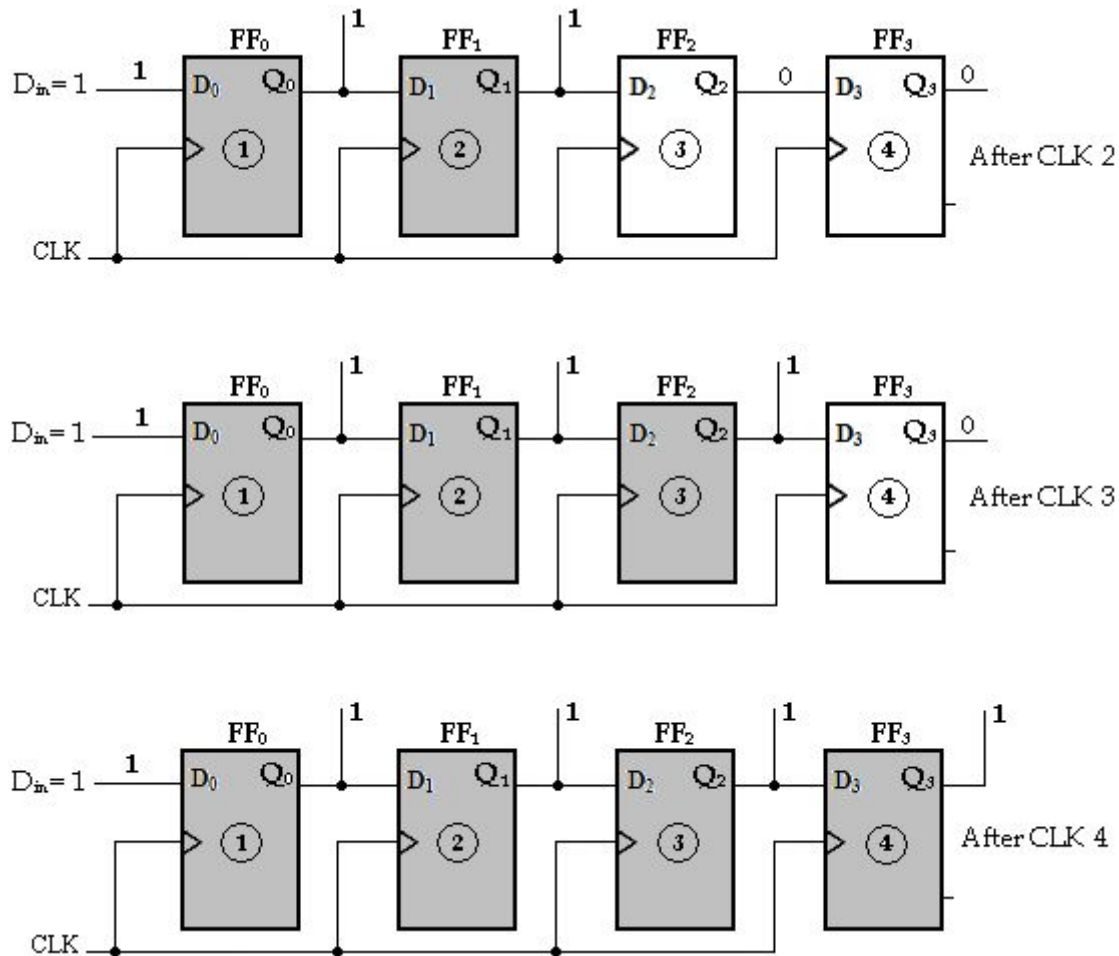

Four bits (1111) being serially entered into the register


## Parallel-In Serial-Out Shift Register:

In this type, the bits are entered in parallel i.e., simultaneously into their respective stages on parallel lines.

A 4-bit parallel-in serial-out shift register is illustrated below. There are four data input lines, X<sub>0</sub>, X<sub>1</sub>, X<sub>2</sub> and X<sub>3</sub> for entering data in parallel into the register. SHIFT/ LOAD input is the control input, which allows four bits of data to **load** in parallel into the register.

When SHIFT/LOAD is LOW, gates G<sub>1</sub>, G<sub>2</sub>, G<sub>3</sub> and G<sub>4</sub> are enabled,

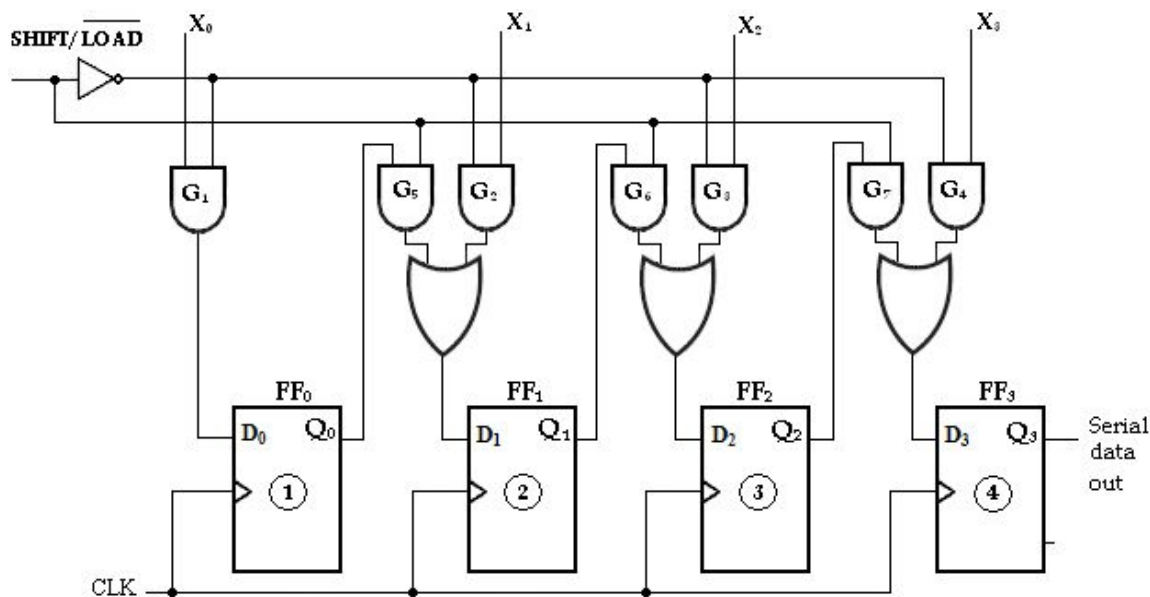allowing each data bit to be applied to the D input of its respective Flip-Flop. When a clock pulse is applied, the Flip-Flops with  $D = 1$  will **set** and those with  $D = 0$  will **reset**, thereby storing all four bits simultaneously.




**Parallel-In Serial-Out Shift Register**

When SHIFT/LOAD is HIGH, gates  $G_1$ ,  $G_2$ ,  $G_3$  and  $G_4$  are disabled and gates  $G_5$ ,  $G_6$  and  $G_7$  are enabled, allowing the data bits to shift right from one stage to the next. The OR gates allow either the normal shifting operation or the parallel data-entry operation, depending on which AND gates are enabled by the level on the SHIFT/LOAD input
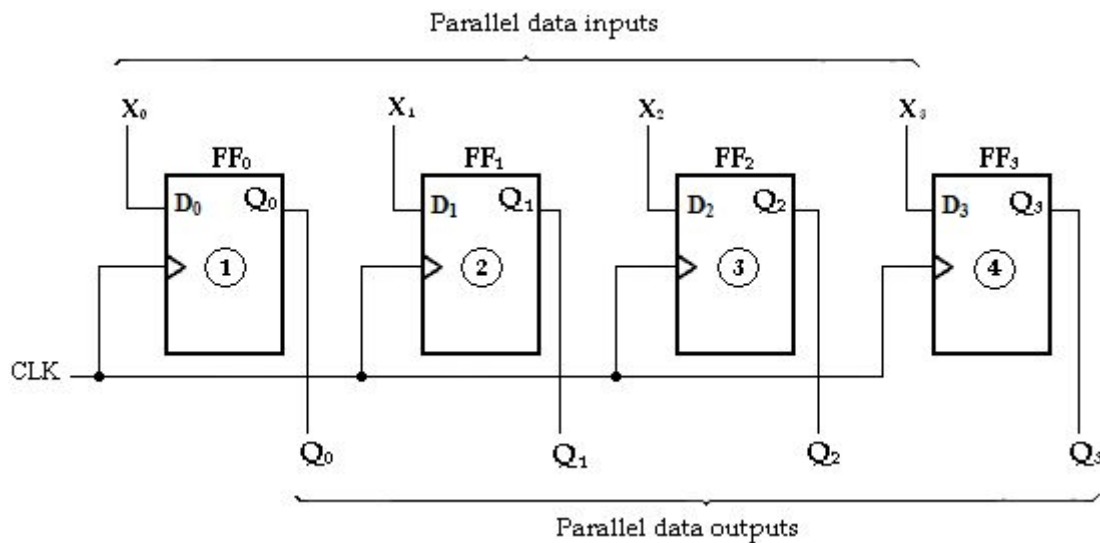
### **Parallel-In Parallel-Out Shift Register:**

In this type, there is simultaneous entry of all data bits and the bits

appear on parallel outputs simultaneously.



**Parallel-In Parallel-Out Shift Register**

## UNIVERSAL SHIFT REGISTERS

If the register has shift and parallel load capabilities, then it is called a shift register with parallel load or **universal shift register**. Shift register can be used for converting serial data to parallel data, and vice-versa. If a parallel load capability is added to a shift register, the data entered in parallel can be taken out in serial fashion by shifting the data stored in the register. The functions of universal shift register are:


- A clear control to clear the register to 0.
- A clock input to synchronize the operations.
- A shift-right control to enable the shift right operation and the serial input and output lines associated with the shift

right.

- A shift-left control to enable the shift left operation and the serial input and output lines associated with the shift left.
- A parallel-load control to enable a parallel transfer and the n input lines associated with the parallel transfer.
- 'n' parallel output lines.
- A control line that leaves the information in the register unchanged even though the clock pulses are continuously applied.

It consists of four D-Flip-Flops and four 4 input multiplexers (MUX).  $S_0$  and  $S_1$  are the two selection inputs connected to all the four multiplexers. These two selection inputs are used to select one of the four inputs of each multiplexer.

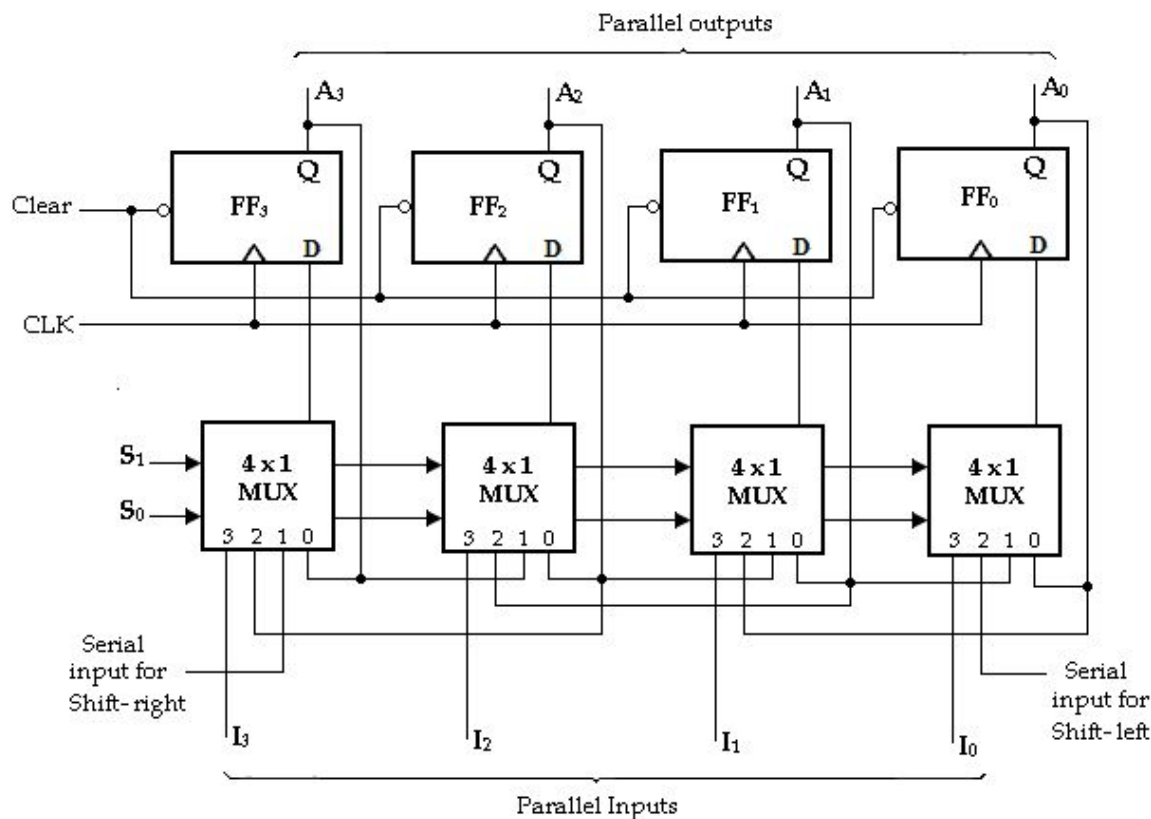The input 0 in each MUX is selected when  $S_1S_0 = 00$  and input 1 is selected when  $S_1S_0 = 01$ . Similarly inputs 2 and 3 are selected when  $S_1S_0 = 10$  and  $S_1S_0 = 11$  respectively. The inputs  $S_1$  and  $S_0$  control the mode of the operation of the register.



#### 4-Bit Universal Shift Register

When  $S_1S_0 = 00$ , the present value of the register is applied to the D-inputs of the Flip-Flops. This is done by connecting the output of each Flip-Flop to the 0 input of the respective multiplexer. The next clock pulse transfers into each Flip-Flop, the binary value is held previously, and hence no change of state occurs.

When  $S_1S_0 = 01$ , terminal 1 of the multiplexer inputs has a path to the D inputs of the Flip-Flops. This causes a shift-right operation with the left serial input transferred into Flip-Flop  $FF_3$ .

When  $S_1S_0 = 10$ , a shift-left operation results with the right serial input going into Flip-Flop  $FF_1$ .

Finally when  $S_1S_0 = 11$ , the binary information on the parallel input lines ( $I_1$ ,  $I_2$ ,  $I_3$  and  $I_4$ ) are transferred into the register simultaneously during the next clock pulse.

The function table of bi-directional shift register with parallel inputs and parallel outputs is shown below.

Mode Control		Operation
S <sub>1</sub>	S <sub>0</sub>	
0	0	No change
0	1	Shift-right
1	0	Shift-left
1	1	Parallel load

## BI-DIRECTIONAL SHIFT REGISTERS:

A bidirectional shift register is one in which the data can be shifted either left or right. It can be implemented by using gating logic that enables the transfer of a data bit from one stage to the next stage to the right or to the left depending on the level of a control line.

A 4-bit bidirectional shift register is shown below. A HIGH on the RIGHT/LEFT control input allows data bits inside the register to be shifted to the right, and a LOW enables data bits inside the register to be shifted to the left.

When the RIGHT/LEFT control input is **HIGH**, gates G<sub>1</sub>, G<sub>2</sub>, G<sub>3</sub> and G<sub>4</sub> are


enabled, and the state of the Q output of each Flip-Flop is passed through to the D input of the following Flip-Flop. When a clock pulse



occurs, the data bits are shifted one place to the right.

When the RIGHT/LEFT control input is **LOW**, gates  $G_5$ ,  $G_6$ ,  $G_7$  and  $G_8$  are

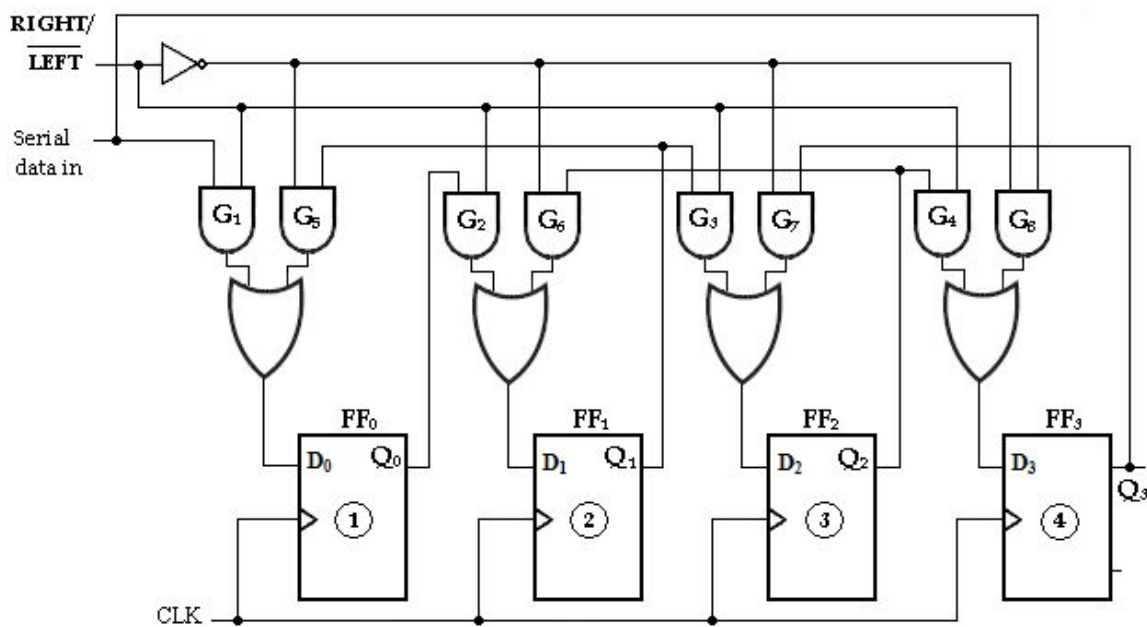enabled, and the Q output of each Flip-Flop is passed through to the D input of the preceding Flip-Flop. When a clock pulse occurs, the data bits are then shifted one place to the left.



4-bit bi-directional shift register

## Shift Register Counter


Shift Register Counters are the shift registers in which the outputs are connected back to the inputs in order to produce particular sequences. These are basically of two types:


### 1. Ring Counter –

A ring counter is basically a shift register counter in which the output of the first flip flop is connected to the next flip flop and so on and the output of the last flip flop is again fed back to the input of the first flip flop, thus the name ring counter. The data pattern within the shift register will circulate as long as clock pulses are applied.

The logic circuit given below shows a Ring Counter. The circuit consists of four D flip-flops which are connected. Since the circuit consists of four flip flops the data pattern will repeat after every four clock pulses as shown in the truth table below:

Clock Pulse	Q1	Q2	Q3	Q4
0	1	0	0	1
1	1	1	0	0
2	0	1	1	0
3	0	0	1	1



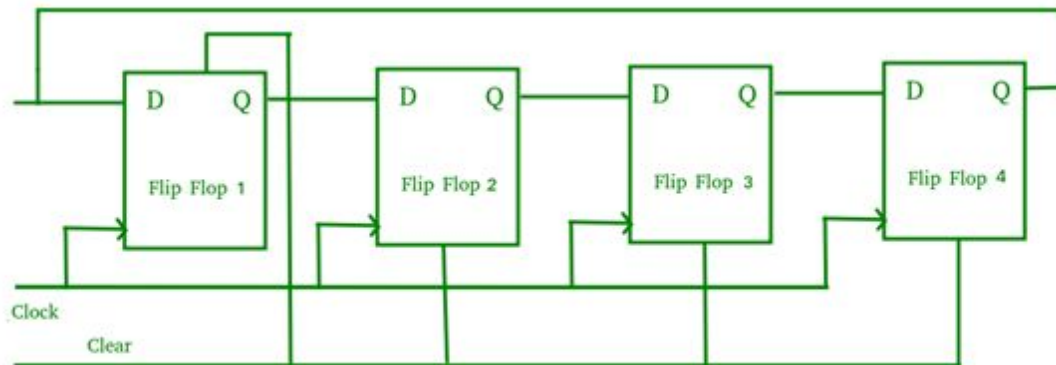


A Ring counter is generally used because it is self-decoding. No extra decoding circuit is needed to determine what state the counter is in.

## 2. Johnson Counter –

A Johnson counter is basically a shift register counter in which the output of the first flip flop is connected to the next flip flop and so on and the inverted output of the last flip flop is again fed back to the input of the first flip flop. They are also known as twisted ring counters.

The logic circuit given below shows a Johnson Counter. The circuit consists of four D flip-flops which are connected. An n-stage Johnson counter yields a count sequence of  $2n$  different states, thus also known as a mod- $2n$  counter. Since the circuit consists of four flip flops the data pattern will repeat every eight clock pulses as shown in the truth table below:

Clock Pulse	Q1	Q2	Q3	Q4
0	0	0	0	1
1	0	0	0	0
2	1	0	0	0
3	1	1	0	0
4	1	1	1	0
5	1	1	1	1
6	0	1	1	1
7	0	0	1	1

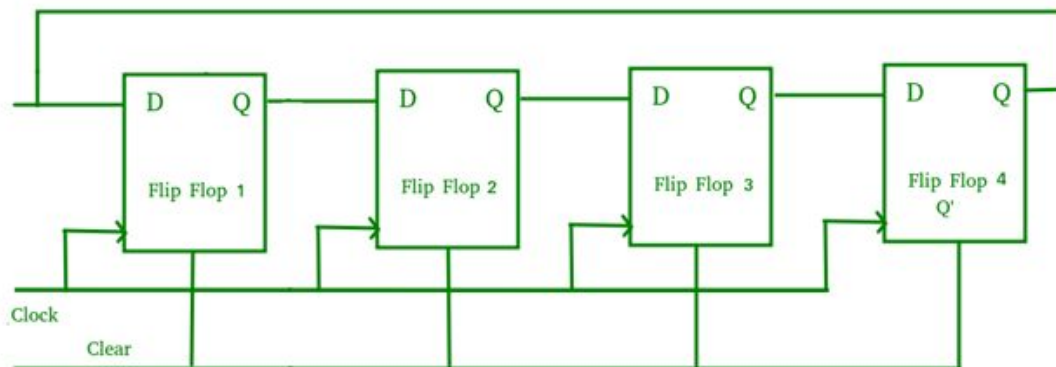

The main advantage of Johnson counter is that it only needs  $n$  number of flip-flops compared to the ring counter to circulate a given data to generate a sequence of  $2n$  states.

