



Sri  
**SAI RAM**  
ENGINEERING COLLEGE  
INSTITUTE OF TECHNOLOGY

West Tambaram, Chennai - 44

YEAR

II

SEM

III

**CS8351**

**DIGITAL PRINCIPLES AND SYSTEM  
DESIGN**

**UNIT NO.2**


**2.4 SUBTRACTOR**

Version: 1.XX


 
### Half -Subtractor:

A half-subtractor is a combinational circuit that can be used to subtract one binary digit from another to produce a DIFFERENCE output and a BORROW output. The BORROW output here specifies




whether a '1' has been borrowed to perform the subtraction.

### Block schematic of half-subtractor

The truth table of half-subtractor, showing all possible input combinations and the corresponding outputs are shown below.

Input		Output	
A	B	Difference (D)	Borrow (Bout)
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0
 
### K-map simplification for half subtractor:



The Boolean expressions for the DIFFERENCE and


BORROW outputs are given by the equations,

Difference,  $D = A'B + AB' = A \oplus B$  Borrow,

$B_{out} = A' \cdot B$

The first one representing the DIFFERENCE (**D**) output is that of an exclusive-OR gate, the expression for the BORROW output (**Bout**) is that of an AND gate with input A complemented before it is fed to the gate.

The logic diagram of the half adder is,

 


### Logic Implementation of Half-Subtractor

Comparing a half-subtractor with a half-adder, we find that the expressions for the SUM and DIFFERENCE outputs are just the same. The expression for BORROW in the case of the half-subtractor is also similar to what we have for CARRY in the case of the half-adder. If the input A, i.e., the minuend is complemented, an AND gate can be used to implement the BORROW output.

Full Subtractor:

A *full subtractor* performs subtraction operation on two bits, a minuend and a subtrahend, and also takes into consideration whether a '1' has already been borrowed by the previous adjacent lower minuend bit or not.

 As a result, there are three bits to be handled at the input of a full subtractor, namely the two bits to be subtracted and a borrow bit designated as  $B_{in}$ . There are two outputs, namely the DIFFERENCE output D and the BORROW output  $B_o$ . The BORROW output bit tells



whether the minuend bit needs to borrow a '1' from the next possible higher minuend bit.

### Block schematic of full-adder

The truth table for full-subtractor is,

Input s			Output s	
A	B	B <sub>in</sub>	Difference(D)	Borrow(B <sub>out</sub> )
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

For Difference

		BB <sub>in</sub>	00	01	11	10
A						
0			0	1	0	1
1			1	0	1	0

For Borrow

		BB <sub>in</sub>	00	01	11	10
A						
0			0	1	1	1
1			0	0	1	0

**Difference, D** =  $A'B'B_{in} + A'BB'_{in} + AB'B'_{in} + ABB_{in}$

**Borrow, B<sub>out</sub>** =  $A'B + A'B_{in} + BB_{in}$


K-map simplification for full-subtractor:

The Boolean expressions for the DIFFERENCE and BORROW outputs are given by the equations,

**Difference, D** =  $A'B'B_{in} + A'BB'_{in} + AB'B'_{in} + ABB_{in}$

**Borrow, B<sub>out</sub>** =  $A'B + A'B_{in} + BB_{in}$  .

 The logic diagram for the above functions is shown as,



### Implementation of full-adder in Sum of Products

The logic diagram of the full-subtractor can also be implemented with two half-subtractors and one OR gate. The difference, D output from the second half subtractor is the exclusive-OR of Bin and the output of the first half-subtractor, giving **Difference**,


$$\begin{aligned}
 D &= \text{Bin} \oplus (A \oplus B) & [x \oplus y &= x'y + xy'] \\
 &= \text{Bin} \oplus (A'B + AB') \\
 &= B'in (A'B + AB') + \text{Bin} (A'B + AB')' & [(x'y + xy')' &= (xy + x'y')] \\
 &= B'in (A'B + AB') + \text{Bin} (AB + A'B') \\
 &= A'BB'in + AB'B'in + ABBin + A'B'Bin .
 \end{aligned}$$

and the borrow output is,

$$\begin{aligned}
 \text{Borrow, Bout} &= A'B + \text{Bin} (A'B + AB')' & [(x'y + xy')' &= (xy + x'y')] \\
 &= A'B + \text{Bin} (AB + A'B') \\
 &= A'B + ABBin + A'B'Bin \\
 &= A'B (\text{Bin} + 1) + ABBin + A'B'Bin & [Cin + 1 &= 1] \\
 &= A'BBin + A'B + ABBin + A'B'Bin \\
 &= A'B + BBin (A + A') + A'B'Bin & [A + A' &= 1] \\
 &= A'B + BBin + A'B'Bin \\
 &= A'B (\text{Bin} + 1) + BBin + A'B'Bin & [Cin + 1 &= 1] \\
 &= A'BBin + A'B + BBin + A'B'Bin \\
 &= A'B + BBin + A'Bin (B + B') \\
 &= A'B + BBin + A'Bin .
 \end{aligned}$$

Therefore,

 we can implement full-subtractor using two half-subtractors and OR gate as,



**Implementation of full-subtractor with two half-subtractors and an OR gate**